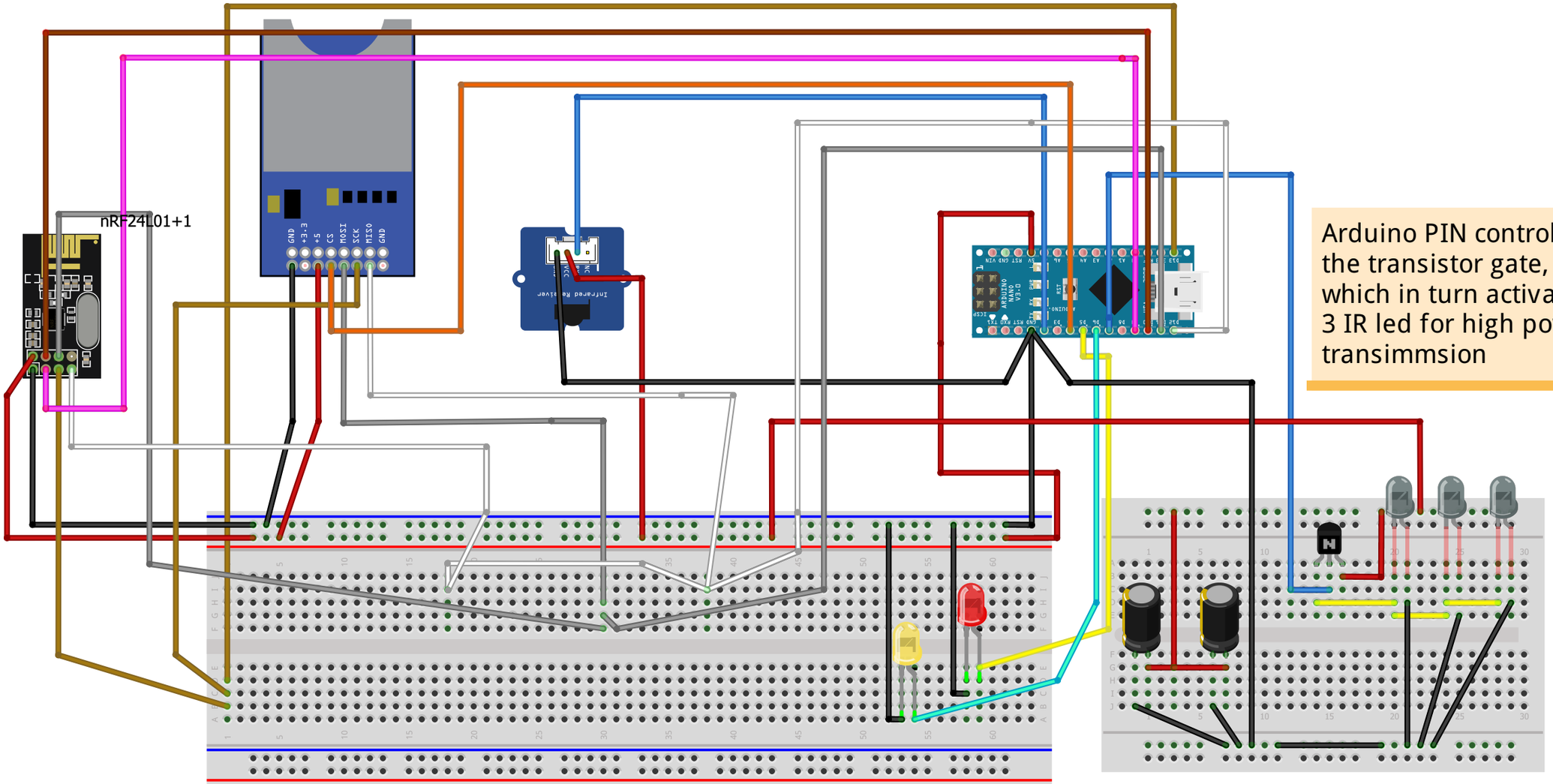

Switches for RF24 once active SPI lines are slaved to the RF24 only and dettached from the SDCard

Switches for SDCard once active SPI lines are slaved to the SDCard only and dettached from the RF24

Collector to device and Emitter to arduino

Optional: For battery usage - the peak current is high - the capacitors will overcome the voltage drop at the peak time and keep the arduino votlage stable (without these it might reset or get stuck)

fritzing